

DC Motor

Overview



This experiment controls the rotation and stop of the DC motor.

Specification Rated Voltage: DC 6V Speed: 5000 RPM

Pin definition

Null

Hardware required


Material diagram	Material name	Number
5	DC Motor	1
	2N3904	1
	IN4148	1
-411)	220/330Ω resistor	1
-(11)	10KΩ resistor	1
	USB Cable	1
	UNO R3	1
	Breadboard	1
	Jumper wires	Several

1



Connection


Schematic

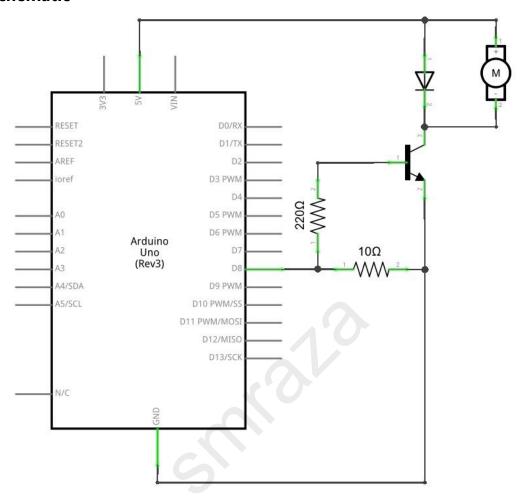

2



Connection diagram

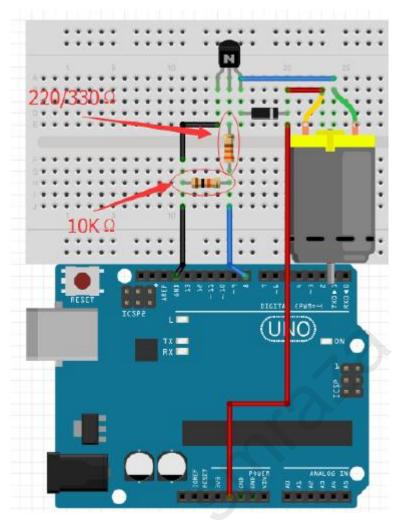

Note:


Pay attention to the direction of the diode(IN4148).



Sample code

```
Note: sample code under the Sample code folder int motor = 8; // motor turn-on trigger signal - active high; void setup (void)
{
    pinMode (motor, OUTPUT); // define port attribute for the output; }
void loop (void)
{
    digitalWrite (motor, HIGH); // delay (1000); digitalWrite (motor, LOW); //switch; delay (1000); }
```

Example picture

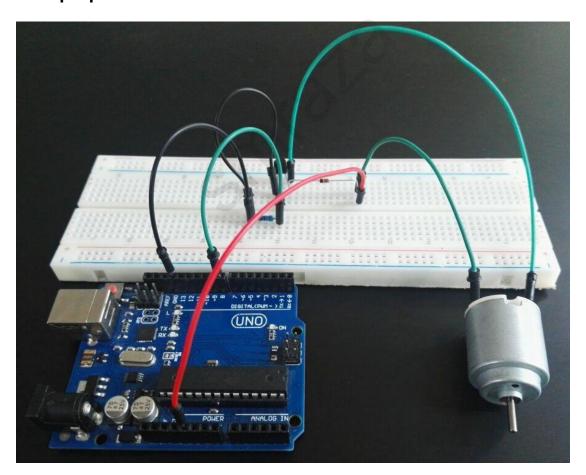



Language reference

Null

Application effect

You'll see the motor stop and turn.

- * About Smraza:
- * We are a leading manufacturer of electronic components for Arduino and Raspberry Pi
- * Official website: http://www.smraza.com/
- * We have a professional engineering team dedicated to providing tutorials and support to help you get started.
- * If you have any technical questions, please feel free to contact our support staff via email at support@smraza.com
- * We truly hope you enjoy the product, for more great products please visit our

Amazon US store: http://www.amazon.com/shops/smraza

Amazon CA store: https://www.amazon.ca/shops/AMIHZKLK542FQ
Amazon UK store: http://www.amazon.co.uk/shops/AVEAJYX3AHG8Q
Amazon DE store: http://www.amazon.de/shops/AVEAJYX3AHG8Q
Amazon IT store: http://www.amazon.it/shops/AVEAJYX3AHG8Q
Amazon ES store: https://www.amazon.es/shops/AVEAJYX3AHG8Q
