


4 digit LED Segment Displays

Overview



This experiment is similar to the LED experiment, the same is the control of LED, but the experiment can achieve time counting function.

Pin definition

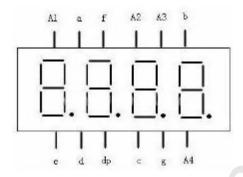


Hardware required

Material diagram	Material name	Number
8.6.B.B.	4 digit LED Segment Displays	1
—(III)—	220/330Ω resistor	8
	USB Cable	1
	MEGA 2560	1
	Breadboard	1
	Jumper wires	Several

1



Connection diagram

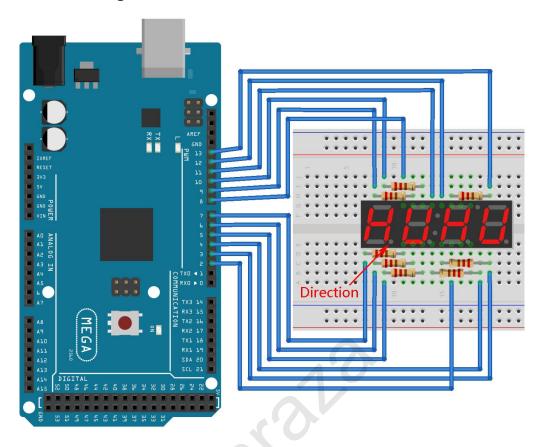

Note: Pay attention to the direction of digital tube.



Sample code

```
Note: sample code under the Sample code folder
int ASeg = 9;
int BSeg = 13;
int CSeg = 4;
int DSeg = 6;
int ESeg = 7;
int FSeg = 10;
int GSeg = 3;
int a1 = 8;
int a2 = 11;
int a3 = 12;
int a4 = 2;
// set variable
long n = 0;
int x = 100;
int del = 54; // fine adjustment for clock
void setup()
{
    pinMode(a1, OUTPUT);
    pinMode(a2, OUTPUT);
    pinMode(a3, OUTPUT);
    pinMode(a4, OUTPUT);
    pinMode(ASeg, OUTPUT);
    pinMode(BSeg, OUTPUT);
    pinMode(CSeg, OUTPUT);
    pinMode(DSeg, OUTPUT);
    pinMode(ESeg, OUTPUT);
    pinMode(FSeg, OUTPUT);
    pinMode(GSeg, OUTPUT);
}
void loop()
{
    clearLEDS(); // Eliminating ghost
    pickDigit(1);
    pickNumber((n/x/1000)%10); // Display number
    delayMicroseconds(del);
    clearLEDS();
    pickDigit(2);
    pickNumber((n/x/100)%10);
    delayMicroseconds(del);
```

smraza

```
clearLEDS();
    pickDigit(3);
    pickNumber((n/x/10)%10);
    delayMicroseconds(del);
    clearLEDS();
    pickDigit(4);
    pickNumber(n/x%10);
    delayMicroseconds(del);
    n++;
}
// Select display position
void pickDigit(int x)
{
    digitalWrite(a1, LOW);
    digitalWrite(a2, LOW);
    digitalWrite(a3, LOW);
    digitalWrite(a4, LOW);
    switch(x)
    {
         case 1:
         digitalWrite(a1, HIGH);
         break;
         case 2:
         digitalWrite(a2, HIGH);
         break;
         case 3:
         digitalWrite(a3, HIGH);
         break;
         case 4:
         digitalWrite(a4, HIGH);
         break;
    }
}
// select display number
void pickNumber(int x)
{
    switch(x) {
    case 1: one(); break;
    case 2: two(); break;
    case 3: three(); break;
    case 4: four(); break;
    case 5: five(); break;
    case 6: six(); break;
    case 7: seven(); break;
```



```
case 8: eight(); break;
    case 9: nine(); break;
    default: zero(); break;
    }
}
void clearLEDS()
{
    digitalWrite(ASeg, HIGH);
    digitalWrite(BSeg, HIGH);
    digitalWrite(CSeg, HIGH);
    digitalWrite(DSeg, HIGH);
    digitalWrite(ESeg, HIGH);
    digitalWrite(FSeg, HIGH);
    digitalWrite(GSeg, HIGH);
}
//Display function '0-9'
void zero() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, LOW);
    digitalWrite(FSeg, LOW);
    digitalWrite(GSeg, HIGH);
}
void one() {
    digitalWrite(ASeg, HIGH);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, HIGH);
    digitalWrite(ESeg, HIGH);
    digitalWrite(FSeg, HIGH);
    digitalWrite(GSeg, HIGH);
}
void two() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, HIGH);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, LOW);
    digitalWrite(FSeg, HIGH);
    digitalWrite(GSeg, LOW);
```

smraza


```
void three() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, HIGH);
    digitalWrite(FSeg, HIGH);
    digitalWrite(GSeg, LOW);
}
void four() {
    digitalWrite(ASeg, HIGH);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, HIGH);
    digitalWrite(ESeg, HIGH);
    digitalWrite(FSeg, LOW);
    digitalWrite(GSeg, LOW);
}
void five() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, HIGH);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, HIGH);
    digitalWrite(FSeg, LOW);
    digitalWrite(GSeg, LOW);
}
void six() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, HIGH);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, LOW);
    digitalWrite(FSeg, LOW);
    digitalWrite(GSeg, LOW);
}
void seven() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, HIGH);
    digitalWrite(ESeg, HIGH);
```



```
digitalWrite(FSeg, HIGH);
    digitalWrite(GSeg, HIGH);
}
void eight() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, LOW);
    digitalWrite(FSeg, LOW);
    digitalWrite(GSeg, LOW);
}
void nine() {
    digitalWrite(ASeg, LOW);
    digitalWrite(BSeg, LOW);
    digitalWrite(CSeg, LOW);
    digitalWrite(DSeg, LOW);
    digitalWrite(ESeg, HIGH);
    digitalWrite(FSeg, LOW);
    digitalWrite(GSeg, LOW);
}
```



Example picture

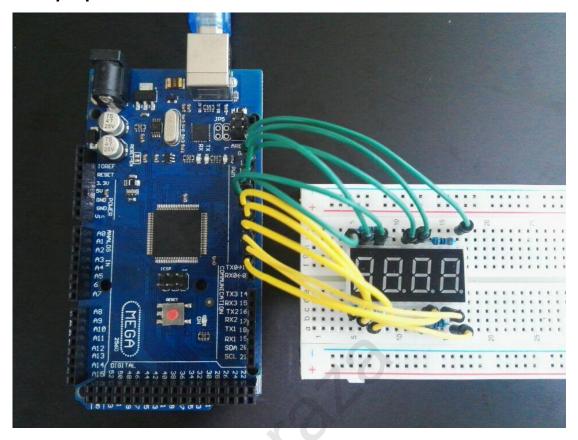



Language reference

Long switch() case

Application effect

In order to achieve the time counting function, you will see the number of digital tube display increasingly.

- * About Smraza:
- * We are a leading manufacturer of electronic components for Arduino and Raspberry Pi.
- * Official website: http://www.smraza.com/
- * We have a professional engineering team dedicated to providing tutorials and support to help you get started.
- * If you have any technical questions, please feel free to contact our support staff via email at support@smraza.com
- * We truly hope you enjoy the product, for more great products please visit our

Amazon US store: http://www.amazon.com/shops/smraza

Amazon CA store: https://www.amazon.ca/shops/AMIHZKLK542FQ
Amazon UK store: http://www.amazon.co.uk/shops/AVEAJYX3AHG8Q
Amazon DE store: http://www.amazon.fr/shops/AVEAJYX3AHG8Q
Amazon IT store: http://www.amazon.it/shops/AVEAJYX3AHG8Q
Amazon ES store: https://www.amazon.es/shops/AVEAJYX3AHG8Q
